

CSSE132

Introduction to Computer Systems

9 : Combinational logic

March 18, 2013

Today: Combinational Logic

- Voting logic and circuit
- Karnaugh maps

- Adding
 - 1-bit adder
 - 32-bit adder
 - Issues with carry

Karnaugh Maps

- Representation of truth table

- Usually 2D
- Axes are input values

- 2 input AND gate example

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

		B	
		0	1
A	0	0	0
	1	0	1

Karnaugh Maps

- Can be extended to 3 and 4 inputs
 - Used to quickly simplify logical expressions
 - Adjacent cells differ by one inversion in product
 - Nearby cells can be grouped into logical expression

		C	
		0	1
AB	00	0	0
	01	0	1
	11	1	1
	10	0	1

		CD			
		00	01	11	10
AB	00	1	0	1	1
	01	0	0	1	1
	11	0	1	1	0
	10	0	1	1	0

K-Map Example

- Logical expression for this truth table
- SOP:
 $A'B'C'D + A'BC'D' + A'BC'D + A'BCD' + A'BCD + ABCD'$
- Simplify with Theorems

A	B	C	D	R
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

K-Map Example

- Build K-map from truth table
 - 2D grid of AB, CD
 - Only change one bit per row/col

A	B	C	D	R
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

K-Map Example

- Build K-map from truth table
 - 2D grid of AB, CD
 - Only change one bit per row/col

		CD			
		00	01	11	10
AB	00	0	1	0	0
	01	1	1	1	1
	11	0	0	0	1
	10	0	0	0	0

A	B	C	D	R
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

K-Map Example

- Group nearby '1's
 - Rectangle shape
 - No 0s inside groups
 - Number of groups cells must be power of two
 - Edges are adjacent
 - Each group must have at least 1 unique cell
 - Each group must be as large as possible
 - Every 1 must be in a group
- Goal: fewest groups possible

		CD			
		00	01	11	10
AB	00	0	1	0	0
	01	1	1	1	1
	11	0	0	0	1
	10	0	0	0	0

K-Map Example

- Group nearby '1's
 - Rectangle shape
 - No 0s inside groups
 - Number of groups cells must be power of two
 - Edges are adjacent
 - Each group must have at least 1 unique cell
 - Each group must be as large as possible
 - Every 1 must be in a group
- Goal: fewest groups possible

		CD			
		00	01	11	10
AB	00	0	1	0	0
	01	1	1	1	1
	11	0	0	0	1
	10	0	0	0	0

K-Map Example

- Form expression from groups
 - SOP expression
- Biggest group:
 - Contains all of CD
 - When A'B
 - = A'B
- Top-left
 - Contains part of C'D
 - Doesn't contain any A
 - = A'C'D
- Rightmost
 - Contains part of CD'
 - Does not contain any B'
 - = BCD'

- SOP:
 $A'B'C'D + A'BC'D' + A'BC'D + A'BCD' + A'BCD + ABCD'$

		CD			
		00	01	11	10
AB	00	0	1	0	0
	01	1	1	1	1
	11	0	0	0	1
	10	0	0	0	0

Majority voting decision

- Returns true when the majority of inputs are true
- What is the K-map?
- What are the groups?
- What is the simplified expression?
- What is the circuit?

A	B	C	R
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Adding

- Binary adder
 - Inputs A and B
 - Outputs sum and carry
- Cannot accept carry
 - Called 'half-adder'
- Expression
 - $S = A'B + AB' = A \oplus B$
 - $C = AB$

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Full-Adder

■ Binary adder

- Inputs A, B, carry
- Outputs sum and carry

■ Expression

- $S = ?$
- $C = ?$

A	B	C	S	C
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Full-Adder

■ Binary adder

- Inputs A, B, carry
- Outputs sum and carry

■ Expression

- $S = ?$
- $C = ?$

A	B	C	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full-Adder

■ Binary adder

- Inputs A, B, C_{in}
- Outputs sum and C_{out}


■ Expression

- $S = AB'C_{in}' + A'BC_{in}' + A'B'C_{in} + ABC_{in}$
- $C_{out} = AB + BC_{in} + AC_{in}$

A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


32 bit adder

 - Abstract 1bit adder to single unit
- Use 32 1bit adders to create 32 bit adder



2 bit adder : 2 x 1 bit adders!

 - Use 2 x 1 bit adders
- Wire C_{out} into next C_{in}
 - Relies on output from previous adder
- Can duplicate for any number of bits




Carry issues

- Consider a 32 bit adder
- Final adder needs input from previous adder (carry result)
- Must wait for 31 other adders!
 - Very slow


$$C1 = (B0 * C0) + (A0 * C0) + (A0 * B0)$$

$$C2 = (B1 * C1) + (A1 * C1) + (A1 * B1)$$

...

 

.....

 

Carry Expansion

- Can represent any function in two levels of logic
 - Build full truth table
 - Construct POS/SOP
 - Implement with gates
- Let's do this for carry

$$c1 = (b0*c0)+(a0*c0)+(a0*b0)$$

$$c2 = (b1*c1)+(a1*c1)+(a1*b1)$$

So...

$$d2 = (b1*(b0*c0)+(a0*c0)+(a0*b0))$$

$$+ (a1 * ((b0*c0)+(a0*c0)+(a0*b0))$$

$$+ (a1*b1)$$

$$c3 = \dots, c4 = \dots$$

- Logic becomes very large
 - Gate/space cost too much

Carry lookahead

- Refactor carry equation
 - Input that generates carry
 - Input that propagates carry
- In general

$$\begin{aligned}c_{i+1} &= (b_i * c_i) + (a_i * c_i) + (a_i * b_i) \\ &= (a_i * b_i) + (a_i + b_i) * c_i\end{aligned}$$

- So, second carry:

$$c_2 = (a_1 * b_1) + (a_1 + b_1) * ((a_0 * b_0) + (a_0 + b_0) * c_0)$$

- In these examples
 - Generate carry: $g_i = (a_i * b_i)$
 - Propagate carry: $p_i = (a_i + b_i) * c_i$

Carry lookahead

■ 4-bit carry lookahead

$$c1 = g0 + (p0 \cdot c0)$$

$$c2 = g1 + (p1 \cdot g0) + (p1 \cdot p0 \cdot c0)$$

$$c3 = g2 + (p2 \cdot g1) + (p2 \cdot p1 \cdot g0) + (p2 \cdot p1 \cdot p0 \cdot c0)$$

$$c4 = g3 + (p3 \cdot g2) + (p3 \cdot p2 \cdot g1) + (p3 \cdot p2 \cdot p1 \cdot g0) + (p3 \cdot p2 \cdot p1 \cdot p0 \cdot c0)$$

■ Build unit that computes carries

- Inputs: $a_0, a_1, a_2, a_3, b_0, b_1, b_2, b_3, \text{carryIn}_0$
- Output: c_1, c_2, c_3, c_4
- Couple with 4-bit adder

■ Each 4-bit adder

- Gets lookahead unit for fast carries

■ To expand beyond 4 bits

- Build carry-lookahead unit for the 4 bit carry-lookahead unit!