

CSSE132

Introduction to Computer Systems

10 : Sequential Logic

March 19, 2013

Today: Sequential Logic

- Sequential logic
- Clocks
- Latches
- Flip-flops
- Build a register file
- Memory


Sequential Logic

■ Combinational logic

- Defined by Boolean expression
- Output based only on input

■ Sequential logic

 - Maintains stored values or state
- Retains data for later use
- Output based on previous input
- Can build state machines




Clock

- **Produce regular changing signal**
 - Special hardware that produces oscillating signal
 - Several waveform outputs
- **Square waveform**
 - Has period (frequency)
 - Duty cycle when power is on
 - Rising edge (power up)
 - Falling edge (power down)
 - Duty cycle often 50% of period
- **Will allow us to transition between states**

Memory circuit

 
- **Two inverter loop**
 - Preserve signal
- **Circuit is hard to use**
 - Can read stored value
 - Can't update stored value
- **Idea is useful**



Memory circuit

■ Build inverter with NAND


- Set inputs to 1
- Same as inverter

 

A	1	X
0	1	1
1	1	0

Memory circuit



- Build loop with NAND
 - Same idea

 

Memory circuit

- **Build loop with NAND**

- Same idea
- Can store 0 or 1

  

Changing value



■ Toggle top input

- Set to 0
- Wait a bit
- Set back to 1

■ What new output if originally

- Top NAND output is 1?
- Top NAND output is 0?

A	B	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0


 
 


Changing value

■ Change top input

- Top input set to 0
- Stored value becomes 1
- 1 value is retained even if input goes to 1

A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

   



Changing value

- Toggle bottom input

- Set to 0
- Wait a bit
- Set back to 1

- Initial value does not matter!

A	B	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0


 
 


Changing value

■ Change bottom input


- Bottom input set to 0
- Stored value becomes 0
- 0 value is retained even if input goes to 1

A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

   

SR Latch

 - **Two inputs, S,R (set, reset)**
 - Change stored value between 1,0
- **Two outputs Q, Q'**
 - Q is stored value
 - Q' must always be opposite of stored value



S'	R'	Q	Q'
0	0	U	U
0	1	1	0
1	0	0	1
1	1	Q_0	Q_0'

Storage cells


- **Many different kinds**
 - Simple ones called 'latches'
 - Bigger, clocked ones called 'flip-flops'
- **Maintain state/stored value**
 - Represented by Q
 - Can transition between states
 - Many conventions
 - Previous/initial state: $Q_0, Q_{\text{prev}}, Q_{t-}$
 - Next state : $Q, Q_{\text{next}}, Q_{t+}$
- **Can have undefined state**
 - Represented by U

Clocked storage

■ D flip-flop


- Has 4 inputs (Data, Set, Reset, Clock)
- Has 2 outputs (Q, Q')
- Changes value on clock edge
 - We will use rising edge

D	Clk	Q	Q'
X	0	Q_0	Q_0'
X	1	Q_0	Q_0'
X	dn	Q_0	Q_0'
0	up	0	1
1	up	1	0

 


Register

 - **Stores binary values**
 - Several flip-flops grouped together
 - Can store 1 bit for each flip-flop
- **Records new value on clock edge**
 - Can be controlled with write-enable bit
- **Allows values to be saved in CPU**
 - Results of calculations
 - Query results from memory
 - Current executing instruction
 - Often word sized



16 bit Register Internal

- 16 D Flip-flops

 



More registers

- **Useful to save several values at once**
 - Multiple register to hold values
- **Give each register/container an ID**
 - Probably a number
- **Useful to select specific register**
 - For reading or writing

Register File

 
- **Collection of registers**
 - **Method to select a single register**
 - Input read or write address
 - **Read or write values**
 - Input write data, output read data
 - **Basic storage unit for CPU**
 - Stores memory fetches
 - Stores calculation results
 - Programmer elects to read or write registers
- ```
put 0xff, reg@2
store reg@3, mem@0xec
add 3, -5, reg@3
```



 

Decoder to select write target

Example 8  
register file

 

Mux to select read output

# Memory

- **Similar to a large register file**
  - Much larger
  - Often slower
- **Address selects byte to manipulate**
  - Read data at byte address
  - Write data at byte address
- **Modern memory**
  - More complex model
  - Hierarchy for read/write
  - Read/writes word size chunks