



CSSE132

Introduction to Computer Systems

11 : Basic computational structures

March 20, 2013

Today: Basic computational structures

■ Helpful structures


- Decoder/encoder
- Multiplexor/demultiplexor
- Sign extender

■ ALU

- ALU control
- Zero detector
- Set less than


Decoder/encoder

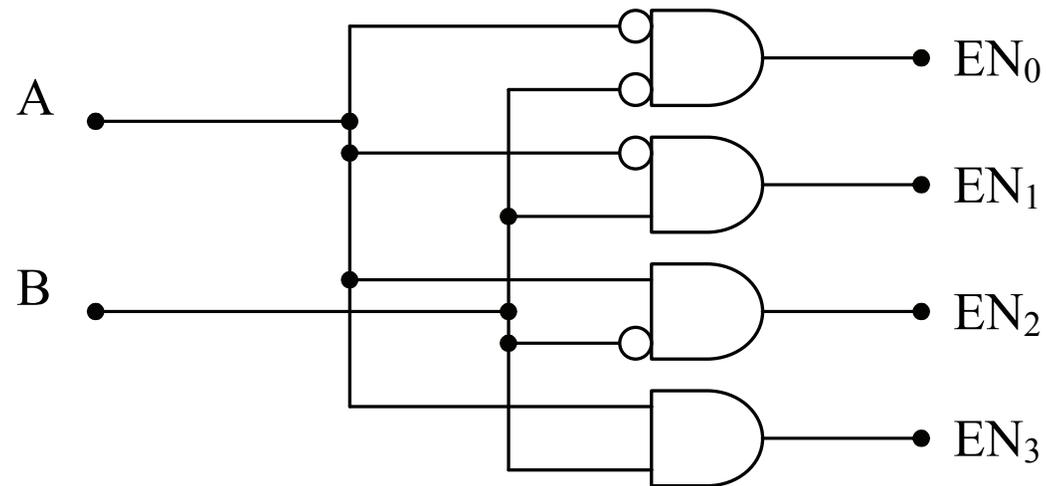- **Outputs unique signal based on input**
 - Inputs: state of systems
 - Output: unique representative code
 - 2 inputs = 2^2 outputs
- **Encoder reverses the process**



Multiplexor

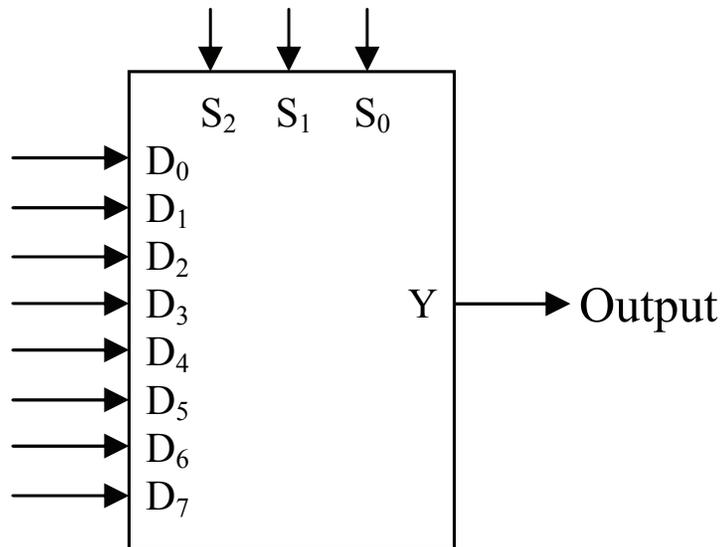
- Select single data stream from multiple channels
 - Multiple data inputs
 - Single data output
 - Control S selects single data stream



S_2	S_1	S_0	Y
0	0	0	D_0
0	0	1	D_1
0	1	0	D_2
0	1	1	D_3
1	0	0	D_4
1	0	1	D_5
1	1	0	D_6
1	1	1	D_7

Demultiplexor

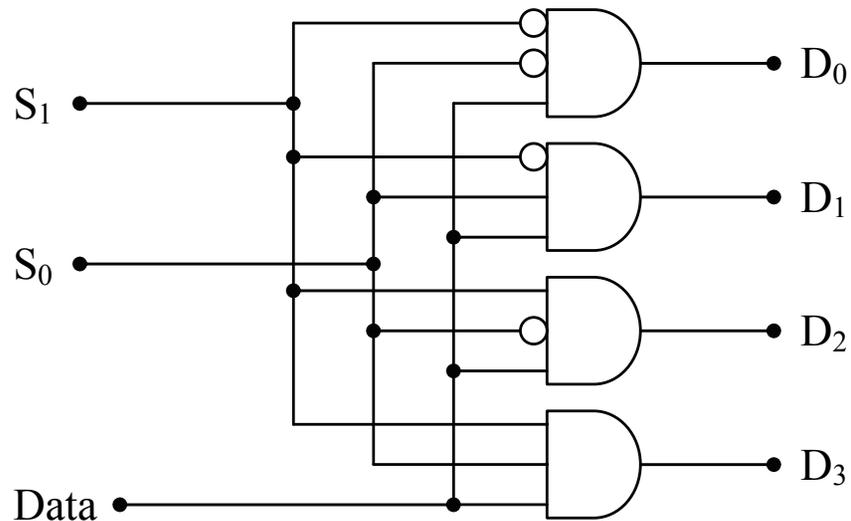- **Outputs data to one of multiple data channels**
 - Single data input
 - Multiple data outputs
 - Control S selects data output



S_1	S_0	Data	D_0	D_1	D_2	D_3
0	0	0	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	0	0
1	0	1	0	0	1	0
1	1	0	0	0	0	0
1	1	1	0	0	0	1

Sign extender

- **CPUs work with signed numbers**
 - Word size or smaller
 - Often need to convert to word size
- **Need to duplicate (extend) sign bit**
 - Preserves original number in larger container
- **How to do this?**

Sign extender

- **CPUs work with signed numbers**
 - Word size or smaller
 - Often need to convert to word size
- **Need to duplicate (extend) sign bit**
 - Preserves original number in larger container
- **How to do this?**
 - Just connect MSB input to sign extend bits!
 - Only need wires

ALU

■ Arithmetic Logic Unit

- Responsible for all computations in computer
- Supported operations
 - AND
 - OR
 - Add
 - Subtract
 - Is less than
 - Is equal
 - Others: NOT, NOR, NAND...
- Design is similar to adder
 - Start with 1 bit ALU, expand

1 bit ALU


- **Start with AND and OR operations**
 - Inputs A and B
 - Select operation by control signal OP
 - Single output R

- **Hint: a multiplexor will help!**
 - Op 0 = AND
 - Op 1 = OR

1 bit ALU

■ Start with AND and OR operations

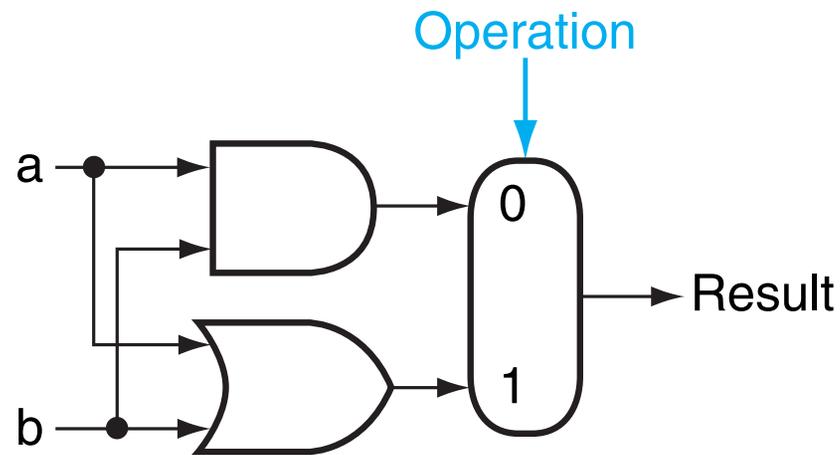- Inputs A and B
- Select operation by control signal OP
- Single output R



1 bit ALU

■ Add in ADD


- We'll use a full adder
- Inputs A, B, C_{in}
- Outputs S, C_{out}
- $S = AB'C_{in}' + A'BC_{in}' + A'B'C_{in} + ABC_{in}$
- $C_{out} = AB + BC_{in} + AC_{in}$

1 bit ALU

■ Add in ADD


- We'll use a full adder
- Inputs A, B, C_{in}
- Outputs S, C_{out}
- $S = AB'C_{in}' + A'BC_{in}' + A'B'C_{in} + ABC_{in}$
- $C_{out} = AB + BC_{in} + AC_{in}$

■ Need to expand mux

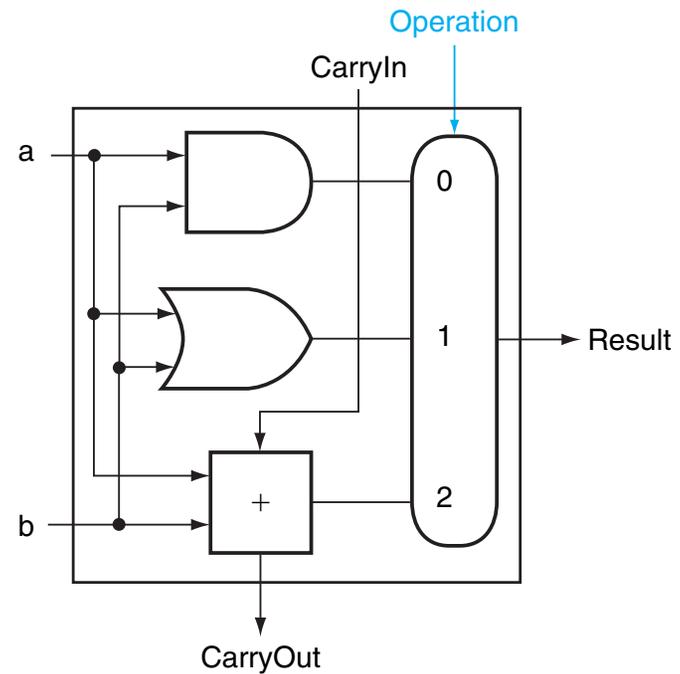

Wider ALU

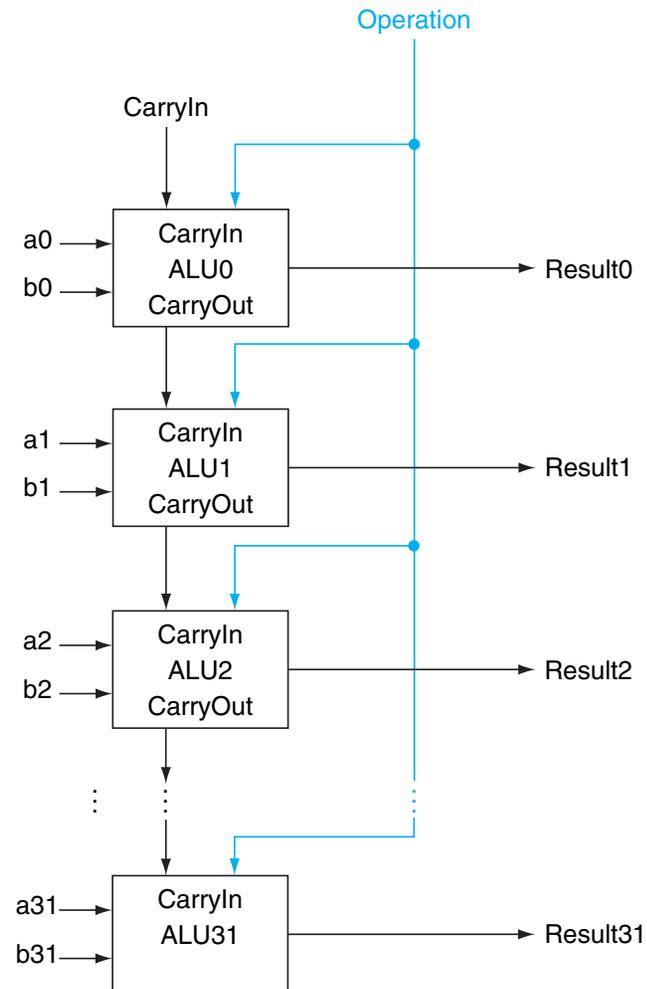- Can link 1 bit ALUs together to form large ALU
 - 32 bit example





Subtract

- Given that 1 bit ALUs form larger ALUs, implement subtract

- Remember Two's complement!

- $-x = (\sim x) + 1$

- What do we need?

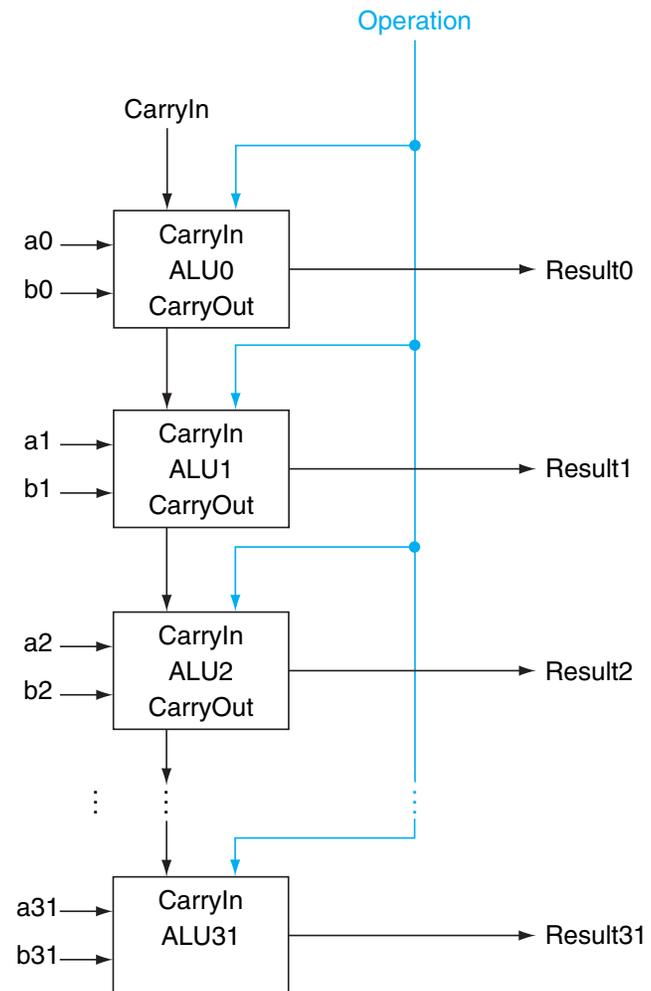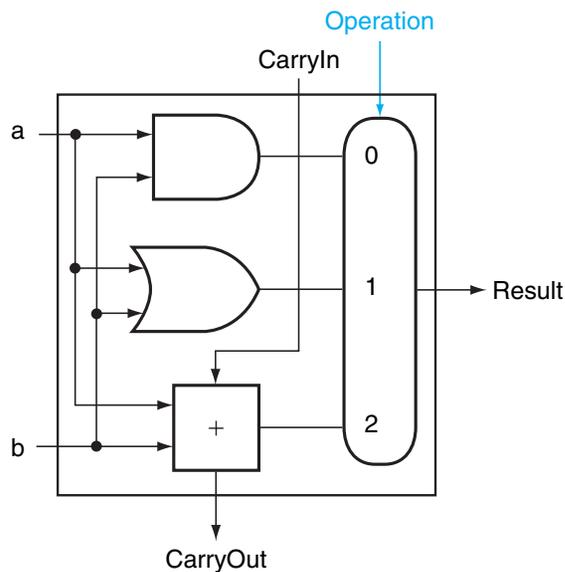



Subtract

- Given that 1 bit ALUs form larger ALUs, implement subtract

- Remember Two's complement!
 - $-x = (\sim x) + 1$

- What do we need?


- Invert B or A
- Add 1 to LSB

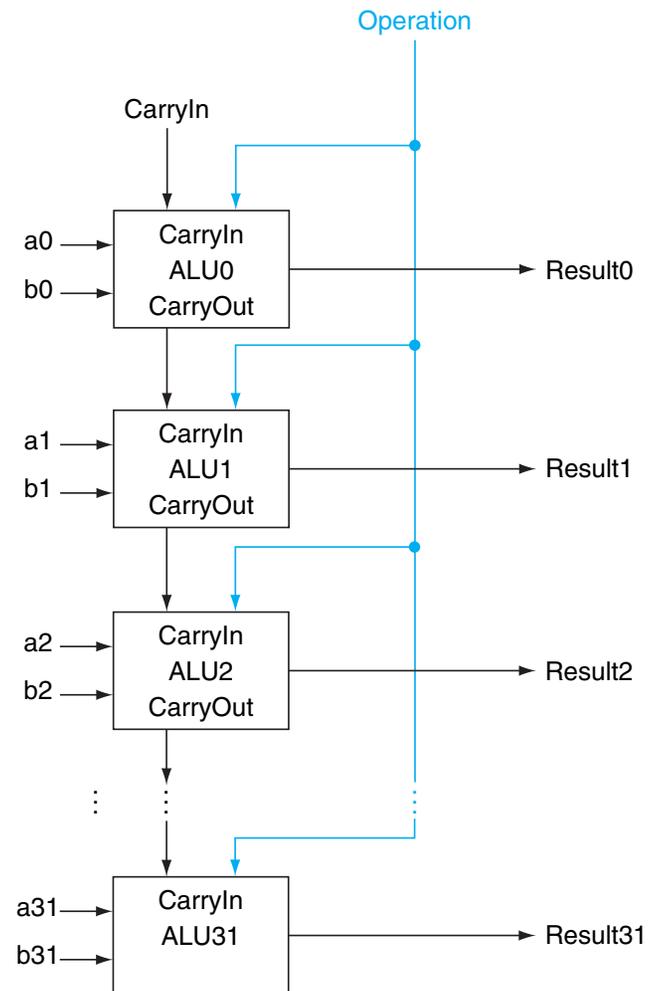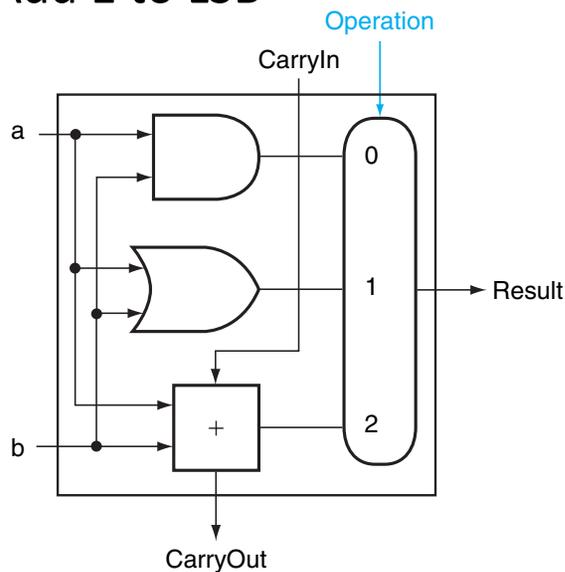

Subtract


■ Invert B

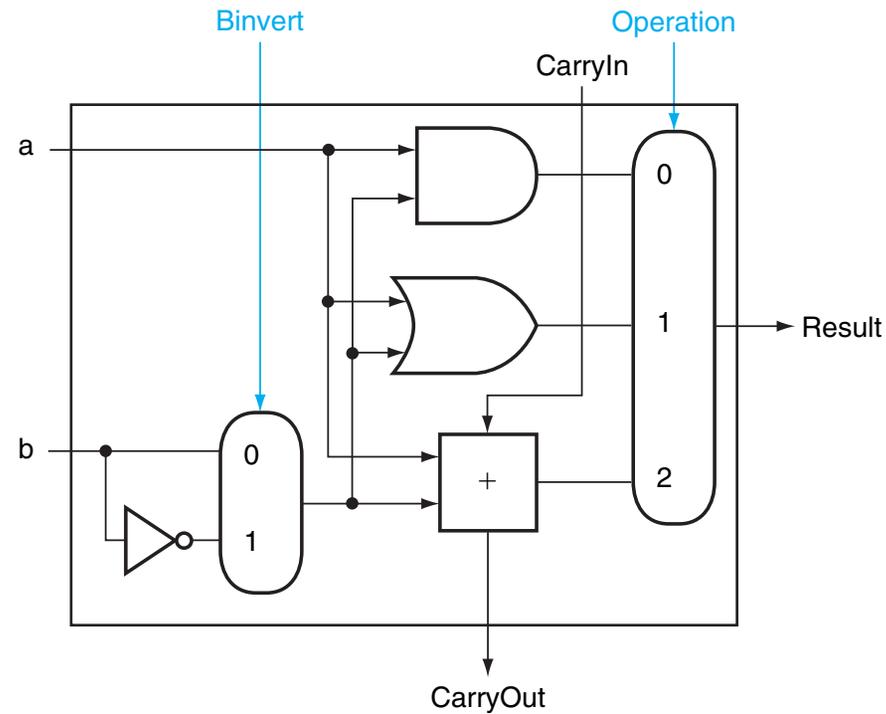- Still need to use adder, so don't expand mux (keep using + op)
- Add control line to select inverted B



Subtract

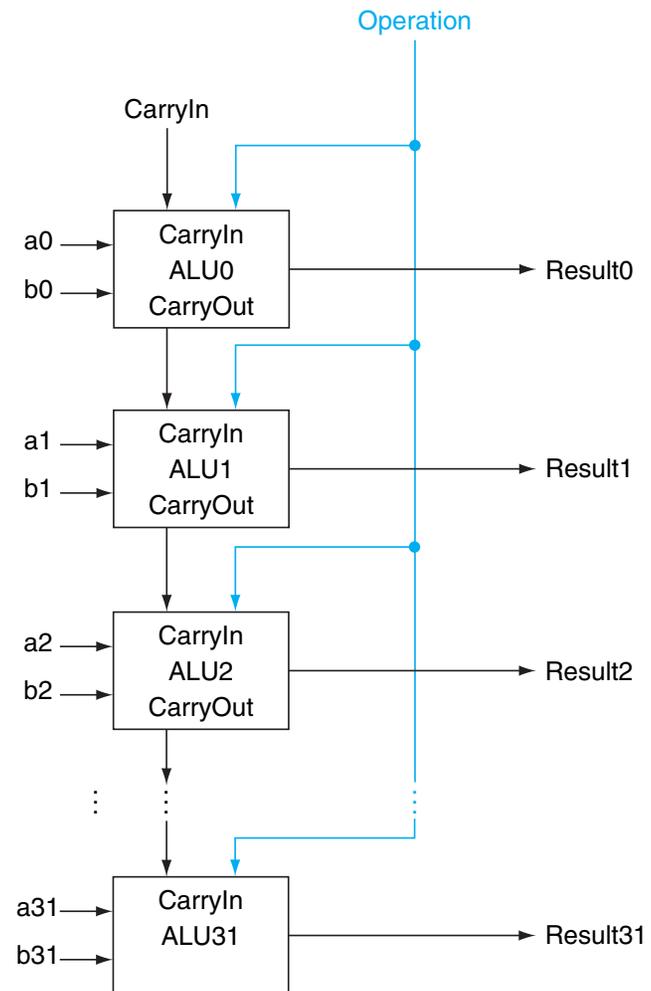- **Add 1 to LSB**
 - If operation is subtract
 - Set LSB carry in to 1
 - Set ALU op to +
- **This incredible convenience is why most computers use two's complement**



Equal


- **Add 1bit 'zero' output to ALU**
 - Set to 1 when A and B are equal
- **How to do?**
 - Subtract A and B
 - If all bits are 0, must be equal!
 - OR all bits
 - Invert result

Other operations

■ Could add more operations

- NOR (invert A)
- Shifting (special hardware)
- Many others...

ALU with NOR support

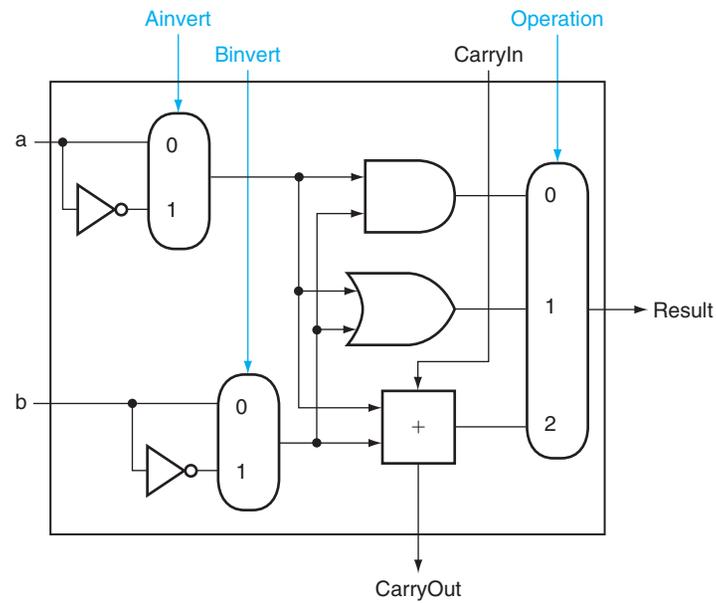

Set less than

- **If $A < B$**
 - $R = 0x00\dots01$
- **If not $A < B$ (i.e. $A \geq B$)**
 - $R = 0x00\dots00$
- **How to do this?**
 - Subtract is useful
 - Sign-bit (MSB) is useful
 - Need to expand mux for new operation

Set less than



- **If $A < B$**
 - $R = 0x00\dots01$
- **If not $A < B$ (i.e. $A \geq B$)**
 - $R = 0x00\dots00$
- **How to do this?**
 - Set LSB to MSB (sign bit)
 - Output 0 for all other bits

Set less than

- **If $A < B$**
 - $R = 0x00\dots01$
- **If not $A < B$ (i.e. $A \geq B$)**
 - $R = 0x00\dots00$

How to do this?

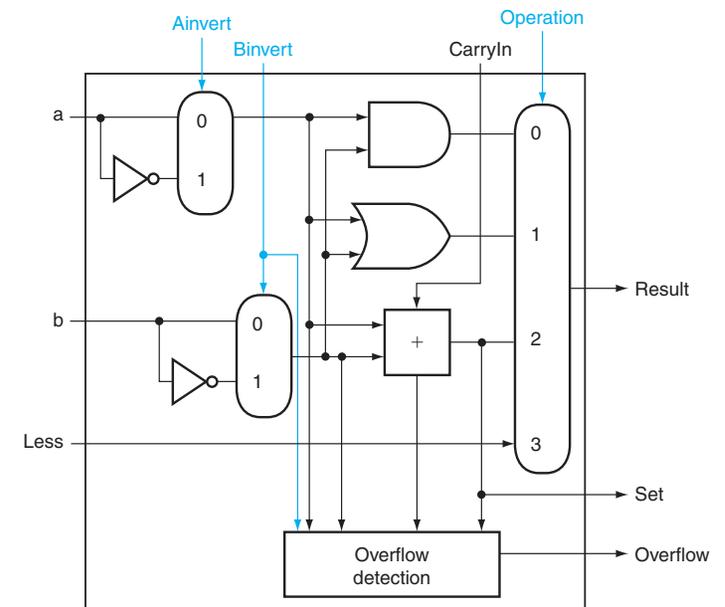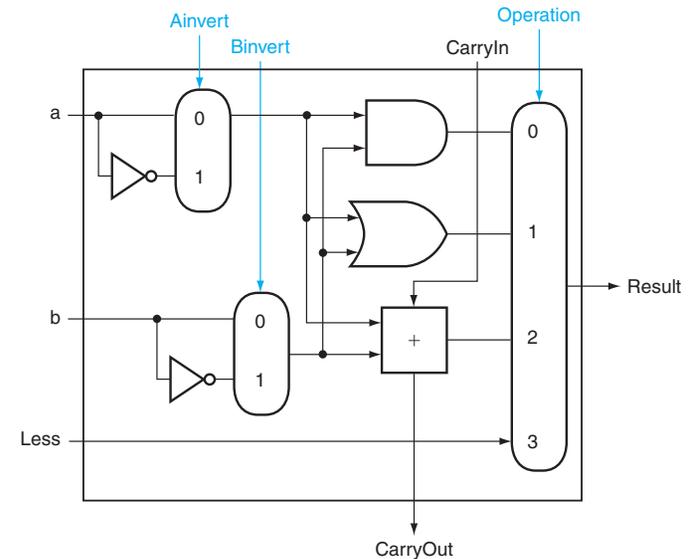- Add new input 'less'
 - Can 0 to result mux
- Add new output 'set' to MSB ALU
 - Output MSB result
 - Use later



Set less than

- **If $A < B$**
 - $R = 0x00\dots01$
- **If not $A < B$ (i.e. $A \geq B$)**
 - $R = 0x00\dots00$
- **Result**
 - Subtract results in < 0
 - Sign bit of 1 is sent to LSB
 - Subtract results in ≥ 0
 - Sign bit of 0 is sent to LSB
 - All other bits set to 0

