

# ECE207 Elements of Electrical Engineering II

Test 1, Fall 2004

Name \_\_\_\_\_

Box # \_\_\_\_\_



For full credit, give units, properly use phasor notation  
and be neat and clear in your solution procedure.

Calculators and an 8½ x 11 sheet (both sides) permitted.

question	possible points	awarded points
1	20	
2	20	
3	20	
4	20	
5	20	
Total	100	

1. The circuit below has its nodes labeled.

 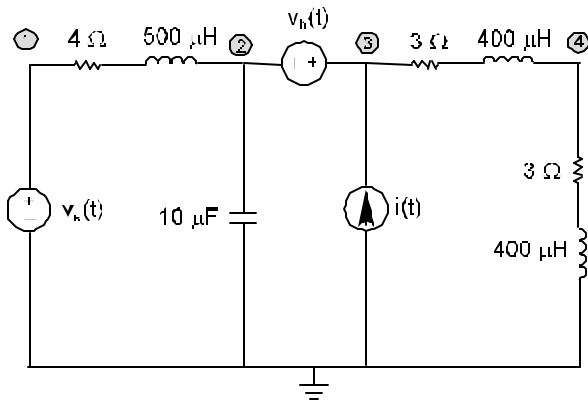i) Give the rms phasor circuit in the space provided given that all sources are 1591.5 Hz and  $v_a(t) = \sqrt{2}(50)\cos(\omega t + 30^\circ)$  V,  $v_b(t) = \sqrt{2}(25)\cos(\omega t - 30^\circ)$  V,  $i(t) = \sqrt{2}(5)\cos(\omega t + 60^\circ)$  A.




ii) List the nodal equations needed to solve for all nodal voltages (DO NOT SOLVE)

2. A trace from an oscilloscope is shown below. The voltage channel was set on 20 V/cm, while the current channel was set on 200 mA/cm. The time-base was set at 2 msec/cm. Determine:

- i) Real power associated with the circuit.
- ii) Reactive power associated with the circuit.
- iii) Apparent power associated with the circuit.
- iv) Frequency (Hz) of the supply.
- v) Impedance of the circuit.
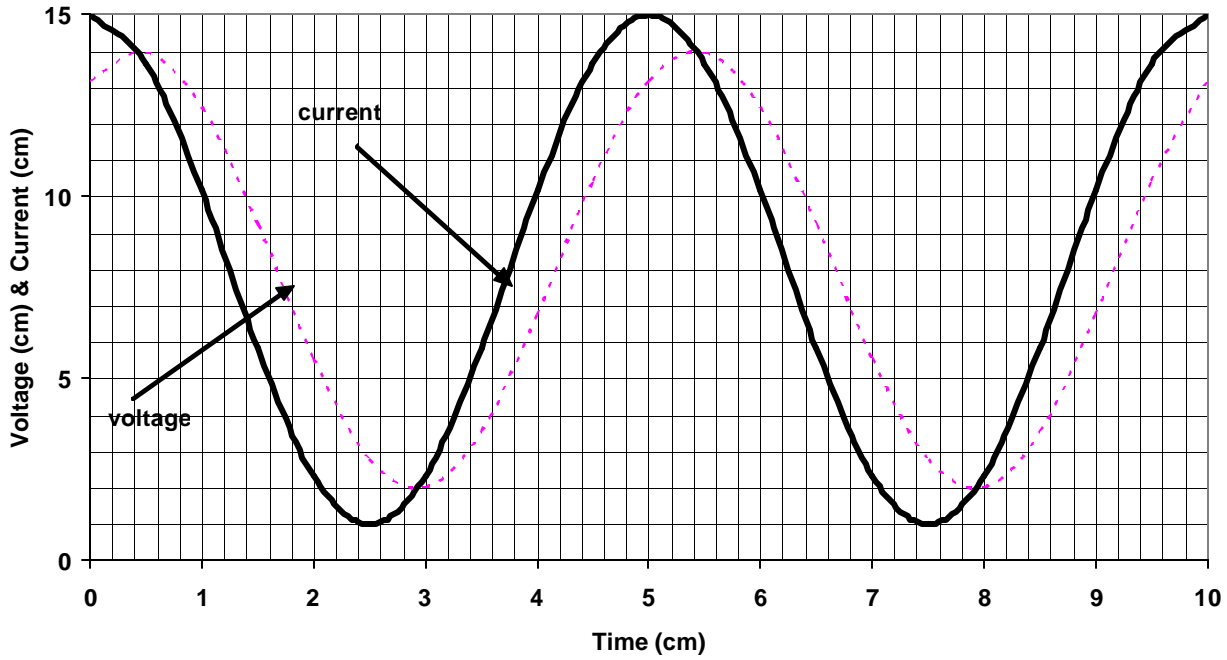
### Oscilloscope Trace of Voltage & Current



3. A single-phase load with an applied voltage of  $v(t)$  and load current of  $i(t)$ , where:

$$v(t) = 5657 \cos(\omega t + 23.1^\circ) \text{ V}$$

$$i(t) = 1768 \cos(\omega t - 13.8^\circ) \text{ A}$$

is connected to a 60 Hz power system. Find:

- i) Voltage and current phasors in terms of rms quantities
- ii) Power triangle with - values of P, Q, S, and  $\phi$  specified
- iii) Capacitance ( $\mu\text{F}$ ) of a capacitor to be connected in parallel with the load to improve the power factor to 0.95 lagging



4. For the system below, there are two loads connected in parallel. Find:

**Load 1**  $(3 + j4) \Omega$


**Load 2**  $30 \text{ kW @ } 0.8 \text{ lag}$

i)  $I$  (5 pts)



ii)  $S_{\text{load}}$  (5 pts)

iii) %VR (5 pts)

iv) % $\eta$  (5 pts)

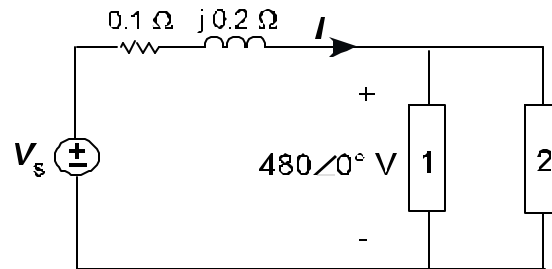

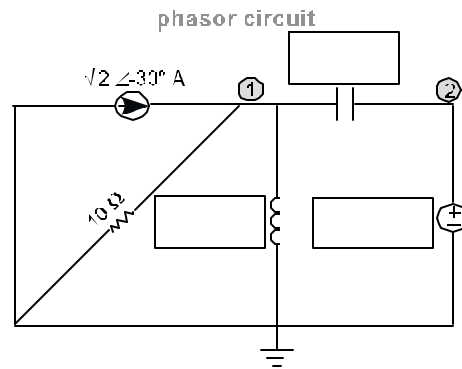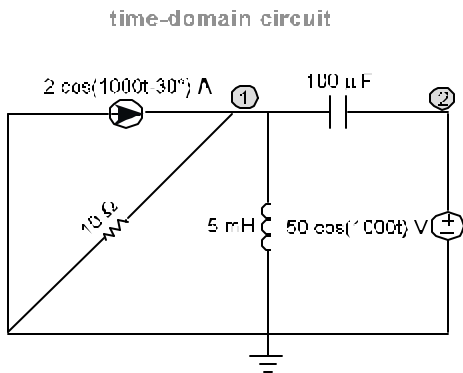5. Check all T/F statements either True or False (T/F) (2 pts each)




for the first three questions

Complete the phasor circuit above.

The complex power delivered by the current source is  $S = V_1 (\sqrt{2} \angle 30^\circ \text{ A})$ .

The sum of the average power delivered by the sources must equal that absorbed by the resistance.

Why or why not? \_\_\_\_\_

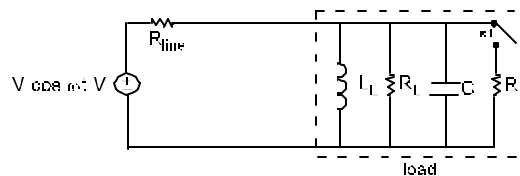

for the next four questions

load impedance is much larger than  $R_{line}$ .


As C is increased from zero (s1 open) the power factor would increase which would lower %VR and raise %η.

Why or why not? \_\_\_\_\_

Closing s1 (C = 0) raises the load power factor and increases the power dissipated in both the load and in  $R_{line}$ .

Increasing  $L_L$  would lower the value of C required to correct the load pf to 1.

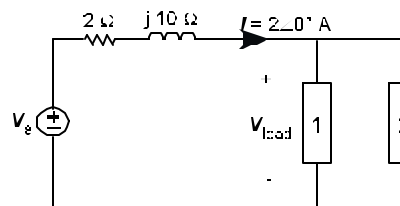For a given  $R_L$  and  $L_L$ , increasing C from zero (s1 open) decreases the line current.



for the next three questions

load 1 =  $150 \angle -53.1^\circ \text{ VA}$   
load 2 = 70 W @ pf=1

$V_{load} = 100 \angle 36.87^\circ \text{ A}$ .

The total average power delivered by the source is 160 W.

Why or why not? \_\_\_\_\_

A power-factor-correction capacitor,  $C_{pfc}$ , in parallel with the loads will increase the load pf, lower the %VR, and increase the system %η.

Why or why not? \_\_\_\_\_

---