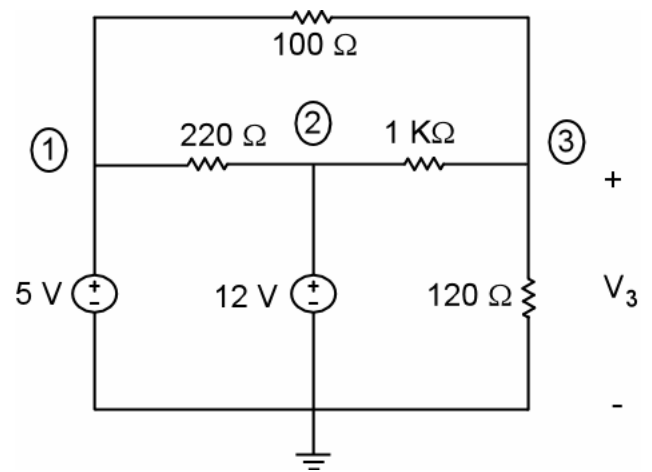


Names _____

Deliverables

- Measured node voltages
- Calculated node voltages using nominal resistance values (attach sheet)
- Calculated node voltages using measured resistance values. (attach sheet)

In the area below, give nodal equations and a list of variables (use nominal values for resistances)



node voltage	measured voltage	calculated (nom. R)	calculated (meas. R)
V_1			
V_2			
V_3			

Nominal R	Measured R
100 Ω	
120 Ω	
220 Ω	
1000 Ω	