### Names \_\_\_

### **Objectives:**

- 1) Design an active low-pass filter with desired LF gain and break frequency.
- 2) Predict magnitude response with hand-drawn Bode plot.
- 3) Compare predictions to MATLAB simulation and laboratory measurements
- 4) Compare predictions to laboratory measurements.

## Deliverables

- 1) Page with detailed design calculations
- 2) Hand-drawn straight-line Bode magnitude plot response predicted from model.
- 3) MATLAB-generated Bode magnitude plot.
- 4) Laboratory measurements of  $V_o/V_s$ .
- 5) Comparison of experimental data to calculated values *AND* to simulation (plot laboratory data on *both* on hand-drawn plot *AND* on MATLAB-generated plot).

# Procedure



- 2. Measure R<sub>in</sub> = \_\_\_\_\_, R<sub>i</sub> = \_\_\_\_\_, and C = \_\_\_\_\_. Use these measured values when calculating model predictions and in producing MATLAB-generated plots.
- 3. Measure the *amplitude* of  $V_0$  for the frequencies indicated below. Adjust amplitude of  $V_s = 1V$  (2V peak-to-peak).

f (Hz)	106	530	1060	2120	10600
Vo					

### **MATLAB Example 1**

$$H(s) = \frac{s+10}{s^2 + 40s + 10000}$$

The MATLAB code for the above transfer function is >> n=[1 10]; >> d=[1 40 10000]; >> h=tf(n,d); ode(h) .

### The resulting plot is shown below



#### **MATLAB Example 1**

MATLAB m-file for a low-pass filter with a transfer function (LP gain=10,  $\omega_b$ =100 r/s.)

$$\mathsf{TF} = \frac{10}{\frac{\mathsf{s}}{100} + 1}$$



