

Names _____

Objectives:

- 1) Develop an understanding of RTDs
- 2) Understand sources of error in temperature measurement with RTDs
- 3) Investigate 2-wire, 3-wire, and 4-wire measurements

Deliverables


- 1) Analysis of 2-wire and 3-wire bridge measurements including an estimation of error.
- 2) Completed procedure

Procedure

2-wire RTD bridge measurement

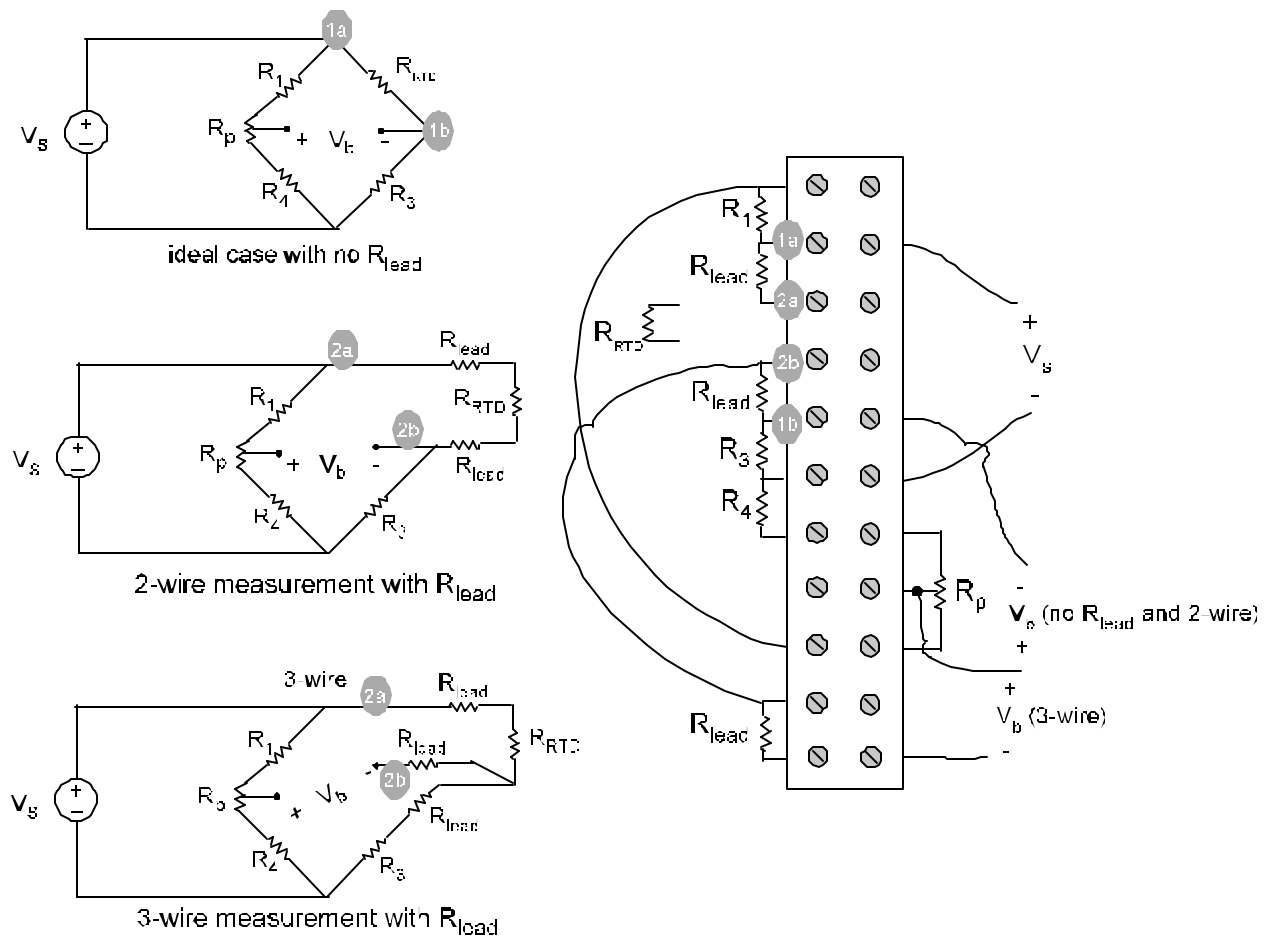1. Build the temperature measurement system shown below.
 $R_1 = R_2 = R_3 = 100 \Omega$, $R_{\text{lead}} = 2.7 \Omega$

schematic for 2-wire and 3-wire RTD laboratory measurements




- With $V_s = 6V$, and the RTD at steady-state temperature in an ice bath, null the bridge with no R_{lead} . (use connections labeled **1** in the diagram above, measure at V_b for no R_{lead}).
- Now, using 2-wire measurement (use connections labeled **2** and V_b at 2-wire), $V_b = \underline{\hspace{2cm}}$ when RTD is in the ice bath.
- Again, using 2-wire measurement, $V_b = \underline{\hspace{2cm}}$ when RTD is at human body temperature.
- Still using 2-wire, $V_b = \underline{\hspace{2cm}}$ when RTD is in boiling water.

3-wire RTD bridge measurement

- With $V_s = 6V$, and the RTD at steady-state temperature in an ice bath, null the bridge with no R_{lead} . (use connections labeled **1** in the diagram above, measure at V_b for no R_{lead}).
- Now, using 3-wire measurement (use connections labeled **2** and V_b at 3-wire), $V_b = \underline{\hspace{2cm}}$ when RTD is in the ice bath.
- Again, using 3-wire measurement, $V_b = \underline{\hspace{2cm}}$ when RTD is at human body temperature.
- Again, using 3-wire, $V_b = \underline{\hspace{2cm}}$ when RTD is in boiling water.

2-wire and 4-wire DMM measurements

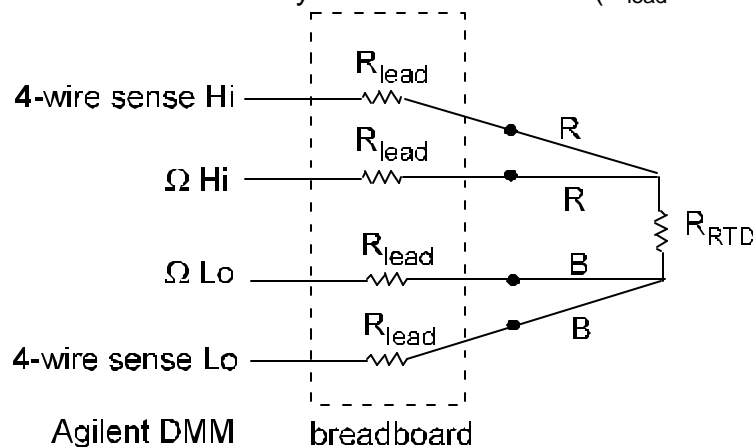- Construct the measurement system shown below. ($R_{lead} = 2.7 \Omega$)



- With the RTD in an ice bath, measure the apparent resistance of the RTD using 2-wire and 4-wire measurements.

$$R_{RTD(2\text{-wire})} = \underline{\hspace{2cm}} \quad R_{RTD(4\text{-wire})} = \underline{\hspace{2cm}}$$

12. With the RTD at human body temperature, measure the apparent resistance of the RTD using 2-wire and 4-wire measurements.

$$R_{\text{RTD}(2\text{-wire})} = \underline{\hspace{2cm}} \quad R_{\text{RTD}(4\text{-wire})} = \underline{\hspace{2cm}}$$

13. With the RTD in boiling water, measure the apparent resistance of the RTD using 2-wire and 4-wire measurements.

$$R_{\text{RTD}(2\text{-wire})} = \underline{\hspace{2cm}} \quad R_{\text{RTD}(4\text{-wire})} = \underline{\hspace{2cm}}$$

Table of temperature measurements

RTDs in lab are all 100Ω platinum with DIN (European) standard RTD characteristics

For this table, record the temperature that corresponds to the apparent RTD resistance. Do not compensate for R_{lead} . For the bridge measurements, measure V_b and then calculate R_{RTD} for the case of $R_{\text{LEAD}} = 0$. For DMM measurements, simply use table to find T corresponding to measured resistance.

	$T_{\text{ice bath}}$	$T_{\text{boiling water}}$	T_{body}
2-wire bridge			
3-wire bridge			
2-wire DMM			
4-wire DMM			

In the areas below, record the actual temperatures extracted corresponding to the true R_{RTD} by properly considering R_{lead} .

A. Calculations for 2-wire RTD bridge measurements

Estimated error caused by not compensating for R_{lead} in temperature measurement using 2-wire RTD bridge measurement.

$$DT_{ice\ bath} = \underline{\hspace{2cm}}$$

$$DT_{body} = \underline{\hspace{2cm}}$$

$$DT_{boiling\ water} = \underline{\hspace{2cm}}$$

B. Calculations for 3-wire RTD bridge measurements

Estimated error caused by not compensating for R_{lead} in temperature measurement using 3-wire RTD bridge measurement.

$$DT_{\text{ice bath}} = \underline{\hspace{2cm}}$$

$$DT_{\text{body}} = \underline{\hspace{2cm}}$$

$$DT_{\text{boiling water}} = \underline{\hspace{2cm}}$$

C. Calculations for 2-wire RTD DMM measurements

Estimated error caused by not compensating for R_{lead} in temperature measurement using 2-wire DMM measurement.

$$DT_{\text{ice bath}} = \underline{\hspace{2cm}}$$

$$DT_{\text{body}} = \underline{\hspace{2cm}}$$

$$DT_{\text{boiling water}} = \underline{\hspace{2cm}}$$