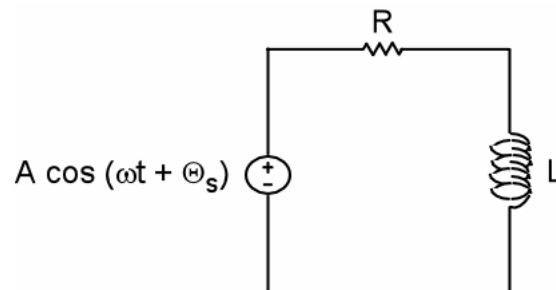


## Sinusoidal steady-state analysis


Phasor analysis is a technique to find the steady-state response when the system input is a sinusoid. That is, phasor analysis is sinusoidal analysis.

Phasor analysis is a powerful technique with which to find the steady-state portion of the complete response. Phasor analysis does **not** find the transient response. Phasor analysis does not find the complete response.


Original circuit



Add an imaginary sine source to obtain

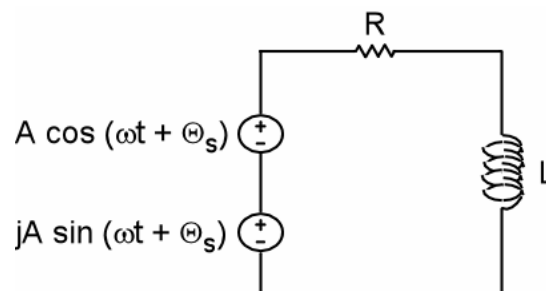

Use Euler's relation to obtain

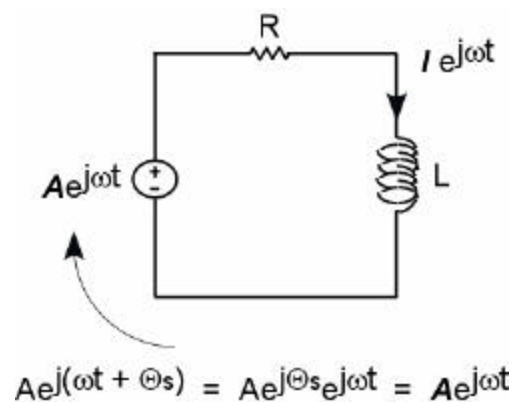

The differential equation becomes

$$R I_L e^{j\omega t} + L d ( I_L e^{j\omega t} )/dt = V_s e^{j\omega t}$$

$$R I_L e^{j\omega t} + j\omega L I_L e^{j\omega t} = V_s e^{j\omega t}$$

$$R I_L + j\omega L I_L = V_s$$

The complex currents and voltages in the equations above are called phasors—phasor currents and phasor voltages.

***Many use the convention of using RMS values when using phasor analysis in electrical circuits. That's what we'll do in this course from now on.***

Notice that, in the equation above, the inductance appears as a "resistance" of  $j\omega L$ . This quantity is referred to as the inductance's impedance.

### Impedance

The algebraic relationship between a phasor voltage and a phasor current is a generalization of resistance and is termed an element's impedance.

The unit of impedance is the ohm.

### Resistance

Let's assume that all the voltages are of the form  $V e^{j\omega t}$  and all the currents are of the form  $I e^{j\omega t}$ .

Let's look at the resistance's element relation, ohm's law.

$$V e^{j\omega t} = R I e^{j\omega t}$$

$$V = R I$$

The impedance of the resistance  $Z_r$  is just its resistance. That is,

$$Z_r = V / I = R$$

## Inductance

From the inductance's element relation:

$$V e^{j\omega t} = L \frac{d(I e^{j\omega t})}{dt} = j\omega L I e^{j\omega t}$$

$$V = j\omega L I$$

$$Z_L = j\omega L$$

## Capacitance

From the capacitance's element relation:

$$I e^{j\omega t} = C \frac{d(V e^{j\omega t})}{dt} = j\omega C V e^{j\omega t}$$

$$I = j\omega C V$$

$$Z_C = 1/j\omega C = -j/\omega C$$


|           | <i>Resistance</i> | <i>Inductance</i> | <i>Capacitance</i>  |
|-----------|-------------------|-------------------|---------------------|
| impedance | $Z_r = R$         | $Z_L = j\omega L$ | $Z_C = -j/\omega C$ |

**Example**

Find  $v_c(t)$  and  $i_x(t)$ .



1. Find phasor circuit (give sources in RMS)
2. Write nodal equations
3. Solve for nodal analysis system
4. Find the phasor voltages and/or currents of interest
5. Use the phasor information to provide the sinusoidal responses.

Time-domain  
circuit

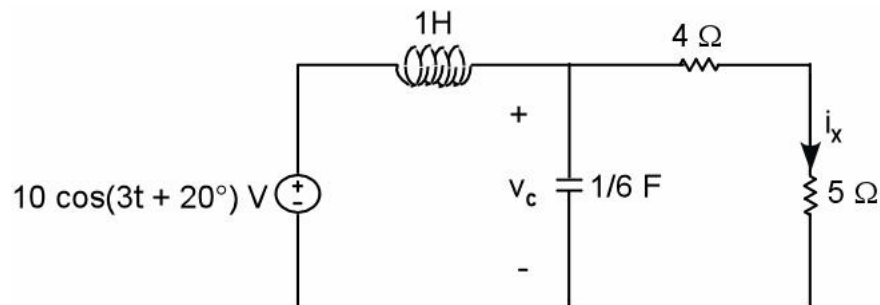

- a) Find phasor circuit
- b) Write the nodal equations to find the phasor voltage across the capacitance,  $V_c$  (express in polar form with the phase in degrees).
- c) Find  $v_c(t)$ , the voltage across the capacitance as a function of time.

Perform nodal analysis on this circuit:

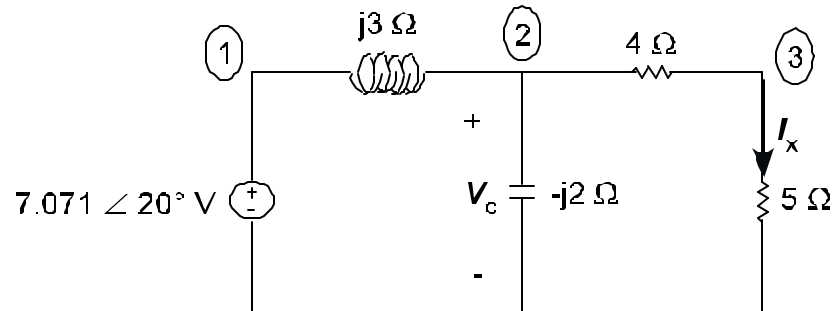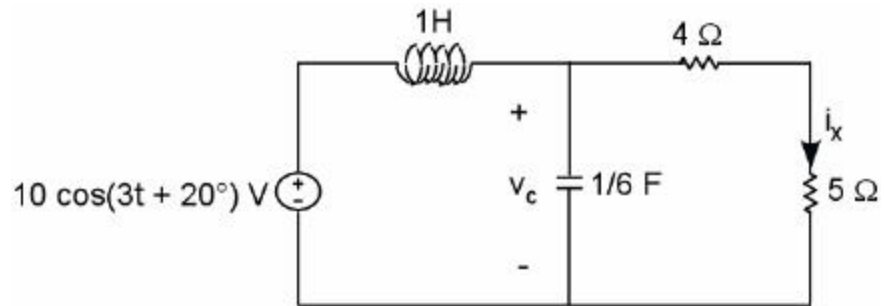

## Using Maple

Phasor analysis example

&gt; restart:

&gt; alias(l='l',j=sqrt(-1)):

&gt; eqns:={v1=7.071\*exp(j\*20\*Pi/180),

&gt; (v2-v1)/(j\*3)+v2/(-j\*2)+(v2-v3)/4=0,

&gt; (v3-v2)/4+v3/5=0};

&gt; soln:=solve(eqns):

&gt; assign(soln):

&gt; vc:=evalf(polar(v2),4);

$$\text{eqns} := \{9/20 v_3 - 1/4 v_2 = 0, v_1 = (10\sqrt{2}) \exp(1/9 j \text{ Pi}),$$

$$- 1/3 j (v_2 - v_1) + 1/2 j v_2 + 1/4 v_2 - 1/4 v_3 = 0\}$$

$$vc := \text{polar}(11.77, -2.205)$$

&gt; evalf(-2.205\*180/Pi,4);

-126.3

check your work:

$$v_c(t) = 11.77 \cos(3t - 126.3^\circ) \text{ V}, \quad i_x(t) = 1.31 \cos(3t - 126.3^\circ) \text{ A}$$

**Discuss**

Again, compare with the big gun technique. How many variables would have been required? How many equations?

**Really good advice on phasor analysis**

Far and away the best tool for phasor analysis is a good engineering calculator. **Experience shows that you will avoid pain, work less, and learn more by taking this simple step.**