

Three-phase power

AC power is typically generated and delivered via 3 ϕ systems. There are two principal advantages to using 3 ϕ power.

1. The power delivered to a balanced 3 ϕ load does not vary with time as do 1 ϕ loads. This results in less vibration and lower stresses in 3 ϕ motors and in systems driven by them.
2. A 3 ϕ system can deliver the same amount of power at lower current levels than can 1 ϕ systems. This allows the use of smaller conductors.

A three-phase source is made from three independent sources. Each of these sources is a sinusoidal source of a certain frequency—all three sources have the same ω , and differing phases—thus the term “three-phase.”

Three-phase source

This 3 ϕ source is connected in the Y-configuration. Here the "Y" can be viewed sideways.


Another 3 ϕ connection, the Δ -configuration, is also possible. For sources, the Y-configuration is most often used.

The source is "balanced" if

$$V_{pa} = V_{pb} = V_{pc} = V_p \quad \text{and if } \theta_a, \theta_b, \text{ and } \theta_c \text{ differ by } 120^\circ$$

If any of these conditions are not met, then the 3 ϕ source is unbalanced.

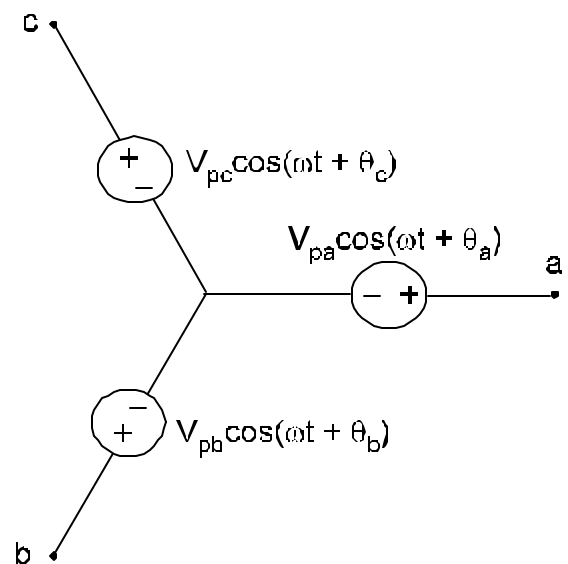To be a balanced 3 ϕ source, the source amplitudes must be equal and their phases must differ from each other by 120°.



Three-Phase Loads

Y-configuration.


The Y-connected 3 ϕ load is said to be "balanced" if all impedances are equal. That is, if $Z_a = Z_b = Z_c = Z_Y$.

If these impedances are not equal, the load is unbalanced.

Δ -configuration.

Likewise, the Δ -connected 3 ϕ load is said to be "balanced" only if all impedances are equal. That is, if $Z_{ab} = Z_{bc} = Z_{ca} = Z_{\Delta}$.

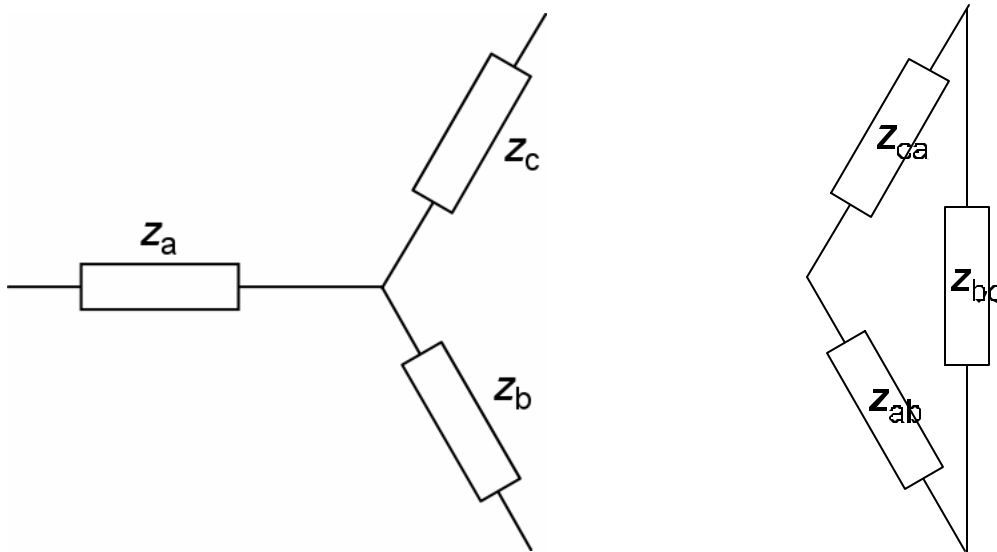If these impedances are not equal, the load is unbalanced.




A balanced 3 ϕ , Δ -connected load can be converted to an equivalent Y-connected load by dividing Z_{Δ} by 3.

A three-phase system—the source and load—is said to be balanced only if both the source and load are balanced. If either is unbalanced, the system is also unbalanced.

- For balanced 3 ϕ systems, we can simplify our task quite a bit if we are familiar with the characteristics of balanced 3 ϕ system.
- On the other hand, the way to treat an unbalanced 3 ϕ system is like any other phasor circuit.

Y-D system

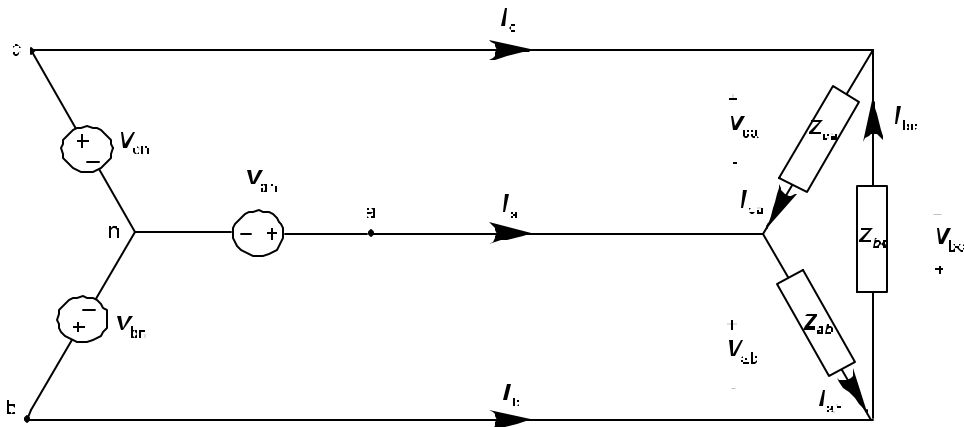

Phase Quantities

Phase currents (I_ϕ) and phase voltages (V_ϕ) are associated with the individual loads and sources

For the Y-connection, the phase currents are I_a , I_b , I_c and the phase voltages are V_{an} , V_{bn} , V_{cn} .

For the Δ -connection, the phase currents are I_{ab} , I_{bc} , I_{ca} and the phase voltages are V_{ab} , V_{bc} , V_{ca} .

Line Quantities

Line currents (I_L) and line voltages (V_L) are the currents in, and the voltages between, the lines between load and source.

They are the same for Y or Δ systems: the line voltages are V_{ab} , V_{bc} , V_{ca} , while the line currents are I_a , I_b , I_c .


In 3ϕ systems, voltages and currents are understood to be line quantities unless otherwise specified. Powers are understood to be 3ϕ powers.

KVL and KCL give the relations between phase quantities and line quantities.

Y: $I_L = I_\phi$

$$V_L = \sqrt{3}V_\phi$$

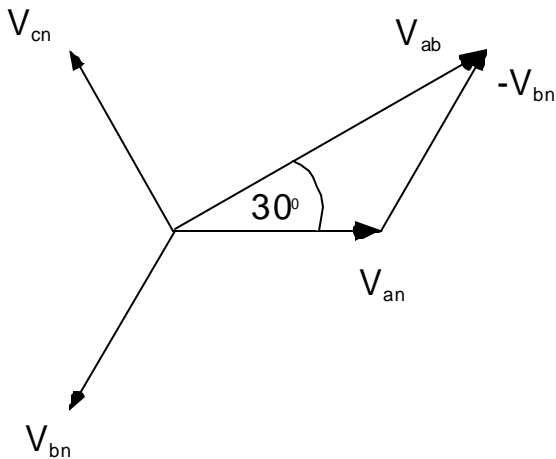the line voltage's phase leads the phase of phase voltages by 30°



KVL gives

$$V_{ab} + V_{bn} - V_{an} = 0$$


Re-arranging gives:

$$V_{ab} = V_{an} - V_{bn}$$

D: $V_L = V_\phi$

$$I_L = \sqrt{3} I_\phi$$

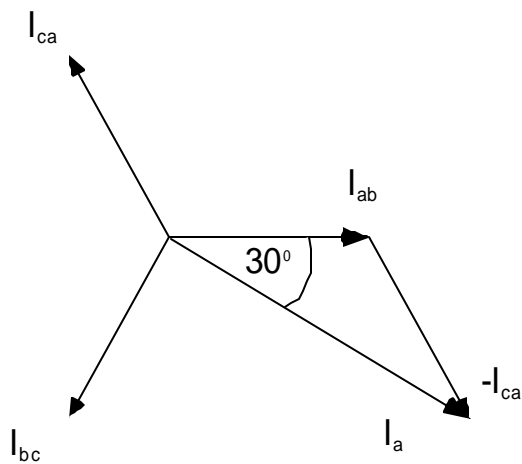the line current's phase lags the phase of phase voltages by 30°



KCL

$$I_a - I_{ab} + I_{ca} = 0$$

Re-arranging gives:

$$I_a = I_{ab} - I_{ca}$$


Example

A 208V 3 ϕ supply feeds a balanced Δ -connected load with

$\mathbf{Z} = 120\angle 35^\circ \Omega$. Determine

- i) the line and phase voltages and currents
- ii) the real, reactive and apparent power supplied to the 3 ϕ load.

Y-Y system

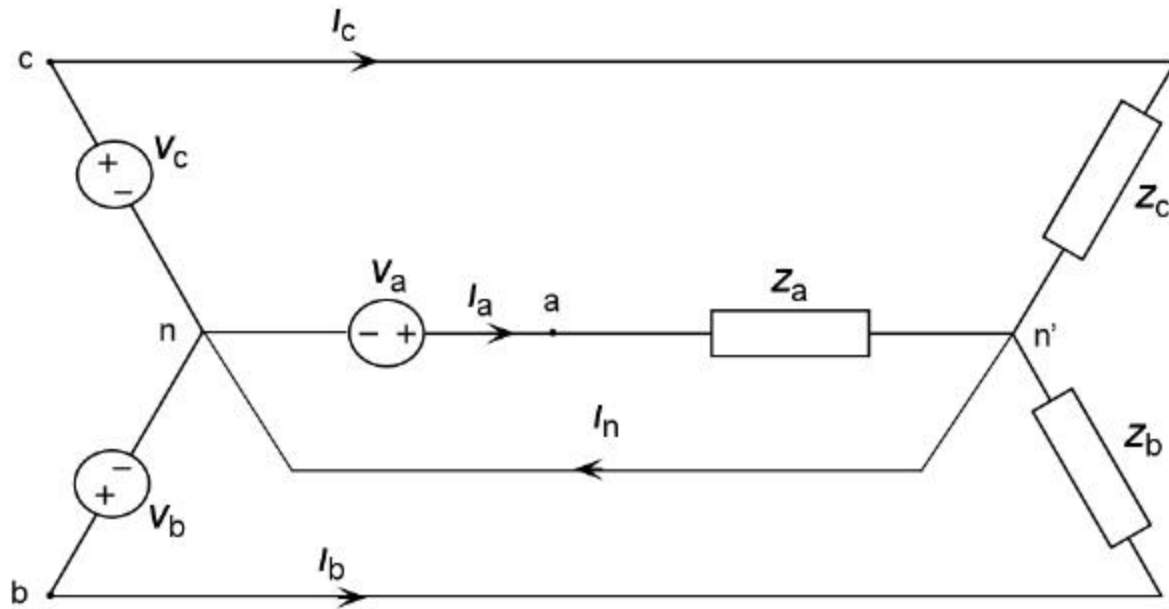


For this to be a balanced system Y-Y 3 ϕ system

1. $Z_a = Z_b = Z_c = Z$
2. The source voltages have the same magnitude and differ 120° in phase.

For a balanced Y-Y system, KCL shows that $I_n = 0$. This is important since the voltage between n and n' must be zero.

The connection between n and n' has no current through it and no voltage across it. **Nothing would be changed if the connection were removed.** In particular, the voltage between n and n' would remain zero even without the connection present.

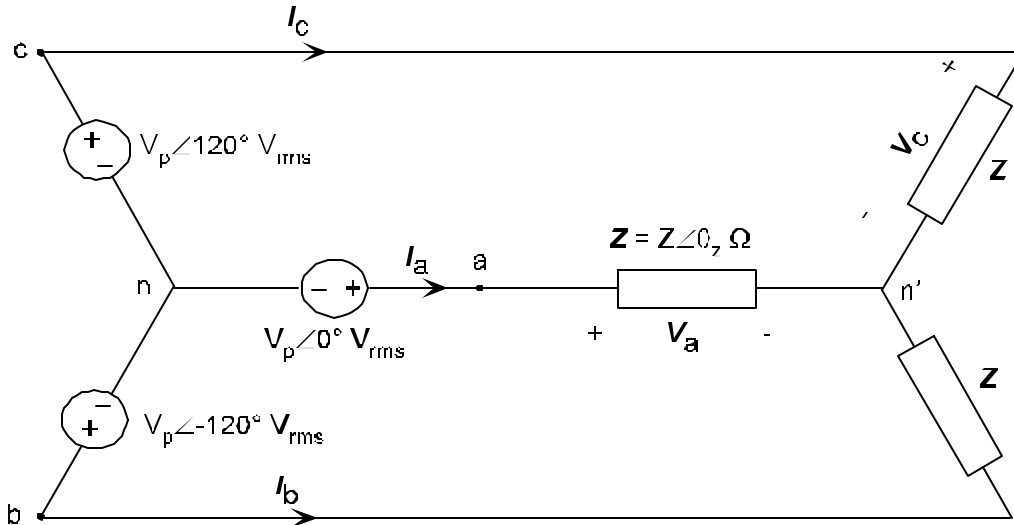Balanced Y-Y System (with neutral connection removed)




Analyzing balanced 3 ϕ systems

1 ϕ equivalent from 3 ϕ

- If loads are given as impedances, convert all Δ s to Y s by dividing Z_{Δ} by 3.
- If loads are given as powers, the powers will be 3 ϕ powers. Divide 3 ϕ power by 3 to obtain 1 ϕ power.
- Divide all line voltages by $\sqrt{3}$ to produce Y phase voltages.
- Analyze the 1 ϕ equivalent system.
- Multiply resulting phase voltages by $\sqrt{3}$ to produce line voltage results.
- Multiply resulting powers by 3 to give 3 ϕ power.

1 ϕ equivalent circuit

Balanced Y-D System

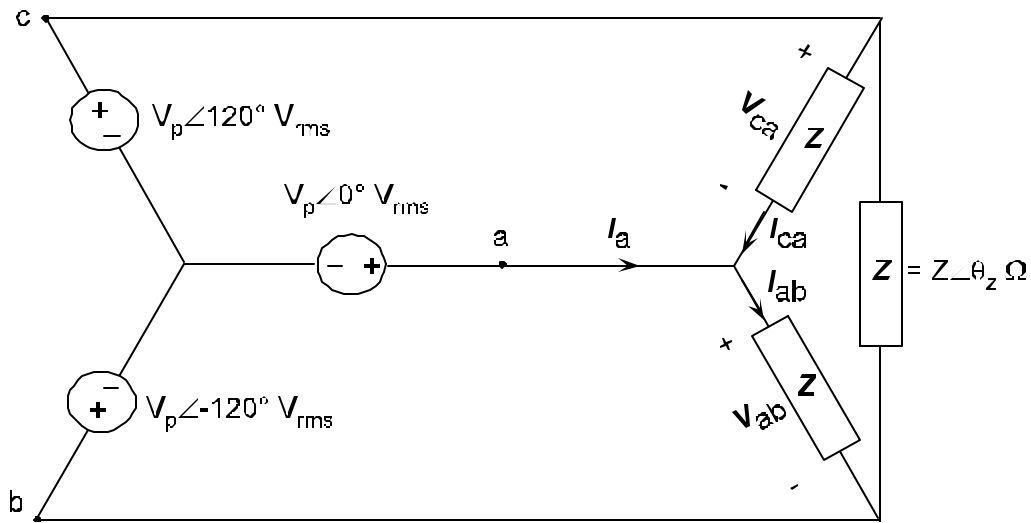1 ϕ equivalent circuit

Example

Two 3 ϕ loads are connected in parallel and supplied at 480 V.

Load 1 is 15 kW, 0.7 lag pf, Y-connected.

Load 2 is 15 kVA, 0.8 lag pf, Δ -connected.

The feeder from the source has an impedance of $0.25 + j0.5 \Omega/\text{phase}$.

Determine

- i) %VR
- ii) P, Q, and S drawn from the source
- iii) pf seen by the source


There are usually two main factors in the cost of electricity:

- i) **Demand charge** which is based on the maximum kVA demanded in the month.
- ii) **Energy charge** which is based on the total kWh consumed in the month.

Electric bills are greatly reduced if the pf is corrected to near unity. It is worth noting that power factors are not corrected to exactly unity because this would lead to the pf being over-correction when the load is small and produce a leading pf.

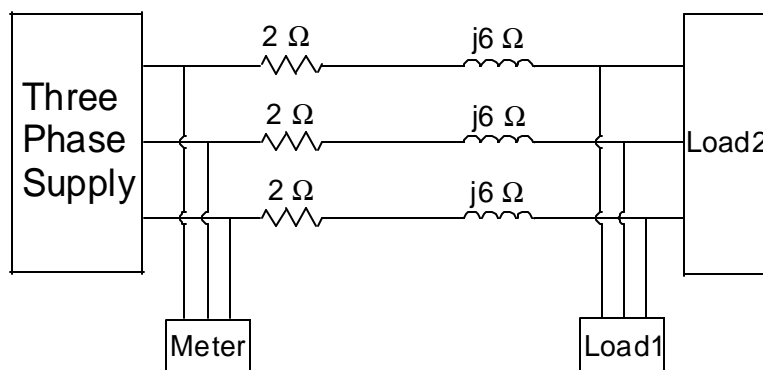Example

The following diagram shows two loads supplied from a common 3 ϕ feeder. Load 1 is 10 MW @ 0.65 lag, while load 2 is 15 MVA @ 0.75 lag. Both loads are supplied at 34.5 kV.



Notice that the meter is placed before the feeder. This means that the feeder losses will be part of the electricity bill.

Determine:

- i) Current in the feeder
- ii) Voltage regulation
- iii) Cost of electricity (\$/yr) for constant loads, energy costs 2.5 ¢/kWh, and demand charge is \$7.00/KVA/mth.
- iv) The capacitance ($\mu\text{F}/\text{ph}$) of a wye-connected capacitor bank needed to improve the combined load pf to 0.98 lag.
- v) Repeat parts (i) - (iii) with the new pf.

General formulas, nomenclature, units, and conventions in power

Time domain


$$v(t) = V_m \cos(\omega t + \theta_v) = V_p \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i) = I_p \cos(\omega t + \theta_i)$$

Phasors with magnitude in peak value

$$\mathbf{V}_p = V_p \angle \theta_v$$

$$\mathbf{I}_p = I_p \angle \theta_i$$

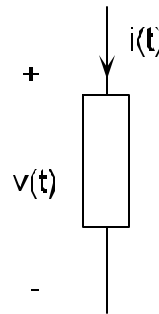

Phasors in rms

$$\mathbf{V} = V \angle \theta_v = (V_p / \sqrt{2}) \angle \theta_v$$

$$\mathbf{I} = I \angle \theta_i = (I_p / \sqrt{2}) \angle \theta_i$$

If a phasor current or voltage is given, without other qualification, it's assumed to be in rms.

Power

$$\mathbf{S} = S \angle (\theta_v - \theta_i) = S \angle \theta_s = P_{av} + jQ$$

\mathbf{S} ~ complex power, in VA

S ~ apparent power, in VA

P_{av} ~ average power, in W

Q ~ reactive power, in VAR

$$\theta_s = \theta_v - \theta_i = \theta_z$$

If power is referred to, without any other qualification, it's assumed to be average power

$$\mathbf{S} = \mathbf{V}\mathbf{I}^* = V \angle \theta_v I \angle -\theta_i = VI \angle (\theta_v - \theta_i) = VI \cos(\theta_v - \theta_i) + j VI \sin(\theta_v - \theta_i)$$

$$S = VI$$

$$P_{av} = VI \cos(\theta_v - \theta_i) = VI \cos \theta_s$$

$$Q = VI \sin(\theta_v - \theta_i) = VI \sin \theta_s$$

$$\text{power factor} = \cos(\theta_v - \theta_i)$$

lagging for $\theta_v > \theta_i$ ($\theta > 0$, $Q > 0$, inductive loads)

leading for $\theta_v < \theta_i$ ($\theta < 0$, $Q < 0$, capacitive loads)

3 ϕ power

- *Unless otherwise specified, voltages and currents are assumed to be line quantities.*
- *Power, unless otherwise specified, is assumed to be average 3 ϕ power.*
- *Any power, unless otherwise specified, is assumed to be 3 ϕ .*

A 3 ϕ system is balanced if

1. Phase voltages are equal in magnitude and displaced 120° in phase from each other.
2. Phase load impedances are equal.

for balanced Y-connection, $V_L = \sqrt{3}V_p$, $I_L = I_p$

for balanced Δ -connection, $V_L = V_p$, $I_L = \sqrt{3}I_p$

$$\theta_s = \theta_z = \theta_v - \theta_i$$

$$\mathbf{S} = S \angle \theta_s = P + jQ$$

$$= \sqrt{3} \mathbf{VI}^* = \sqrt{3} VI \cos \theta_s + j\sqrt{3} VI \sin \theta_s$$