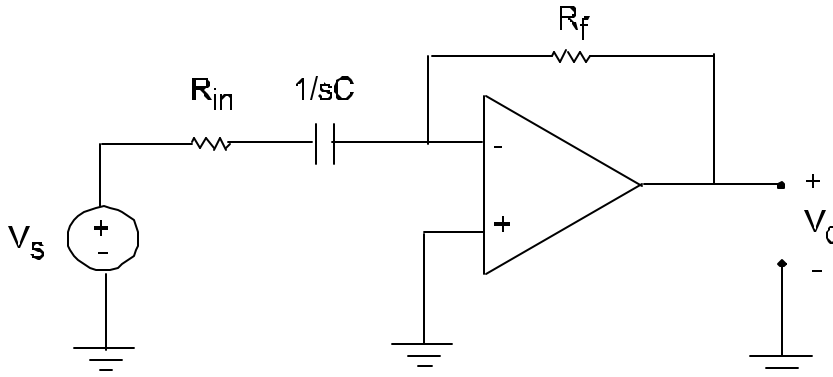


## Frequency Response

### High Pass

This filter has a break frequency (in rad/s),  $\omega_b = 1/R_{in}C$  and a high frequency (HF) gain of  $-R_f/R_{in}$ .



$$\frac{V_o}{V_s} = -\frac{Z_f}{Z_{in}} = -\frac{R_f}{(sR_{in}C + 1) / sC} = -\frac{sR_fC}{sR_{in}C + 1}$$

### Example


A 2V amplitude sinusoidal signal at 20 kHz is corrupted by a 4V noise signal at 120 Hz. Design a HP filter with a HP gain of 3 that significantly attenuates the noise signal.

HP example (cont.)
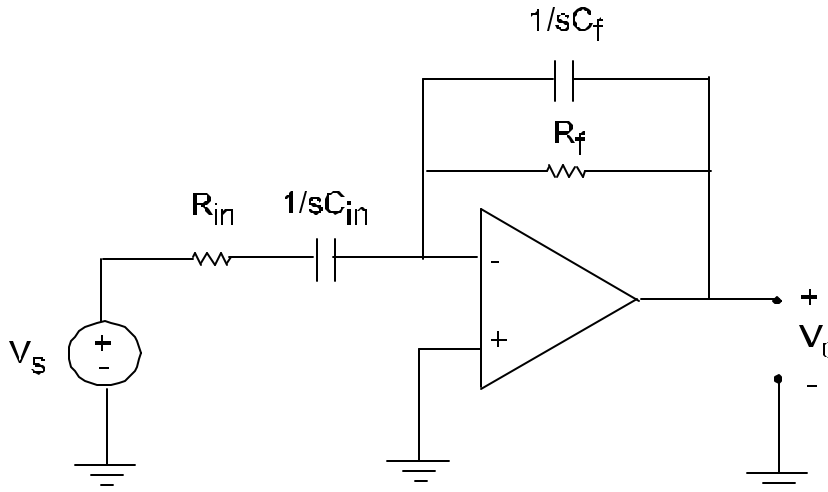
## Band Pass

Bandpass filters are useful when we wish to pass a band of frequencies while, at the same time, we wish to attenuate lower and higher frequencies.

Active bandpass filters, like the one shown below, can not only filter unwanted frequencies, but can amplify signals in a band of frequencies (frequencies in the “pass band.”)



### General analysis

$$\frac{V_o}{V_s} = -\frac{Z_f}{Z_{in}} = -\frac{R_f / (sR_f C_f + 1)}{(sR_{in} C_{in} + 1) / sC_{in}} = -\frac{sR_f C_{in}}{s^2 R_f R_{in} C_f C_{in} + s(R_f C_f + R_{in} C_{in}) + 1}$$

$$\frac{V_o}{V_s} = -\frac{sR_f C_{in} / R_f R_{in} C_f C_{in}}{s^2 + s\left(\frac{R_f C_f + R_{in} C_{in}}{R_f R_{in} C_f C_{in}}\right) + \frac{1}{R_f R_{in} C_f C_{in}}}$$

where  $\frac{1}{R_f R_{in} C_f C_{in}} = \omega_n^2$  and  $\frac{R_f C_f + R_{in} C_{in}}{R_f R_{in} C_f C_{in}} = \omega_{hp}$ , the half-power bandwidth

$$\text{at } s = j\omega = j\omega_n, \quad \frac{V_o}{V_s} = -\frac{j\omega_n R_f C_{in} / R_f R_{in} C_f C_{in}}{j\omega_n \left(\frac{R_f C_f + R_{in} C_{in}}{R_f R_{in} C_f C_{in}}\right)} = -\frac{R_f C_{in}}{R_f C_f + R_{in} C_{in}}$$

$R_{in}C_{in} \gg R_fC_f$

When  $R_{in}C_{in} \gg R_fC_f$ , we obtain significant simplifications.

1<sup>st</sup>, the lower corner frequency,  $\omega_L$ , can be approximated entirely in terms of  $R_{in}$  and  $C_{in}$ .

$$\omega_L \cong \frac{1}{R_{in}C_{in}}$$

2<sup>nd</sup>, the upper corner frequency,  $\omega_u$ , can be approximated entirely in terms of  $R_f$  and  $C_f$ .

$$\omega_u \cong \frac{1}{R_fC_f}$$

3<sup>rd</sup>, the resonant frequency,  $\omega_n$ , is geometric mean of  $\omega_L$  and  $\omega_u$ .

$$\omega_n = \sqrt{\omega_L \omega_u} = \sqrt{\frac{1}{R_{in}C_{in}R_fC_f}}$$

Finally, the gain at resonance is  $-R_f/R_{in}$ .

$$\frac{V_0}{V_s} = -\frac{R_fC_{in}}{R_fC_f + R_{in}C_{in}} = -\frac{R_fC_{in}}{R_{in}C_{in}} = -\frac{R_f}{R_{in}}$$

### Example

A signal, 2V peak-to-peak, at 2.4 kHz is corrupted by 10V peak-to-peak LF noise at 60 Hz and by 5V peak-to-peak HF noise at 20 kHz.

Design a BP filter with a passband gain of 10 that significantly attenuates the LF and HF noise.

BP example (cont.)