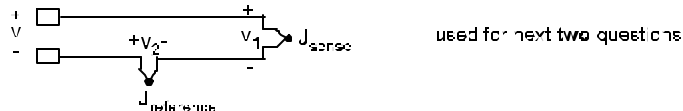


Mark **each** true/false question either **T** OR **F** (1pt each)

___ (**numeric**) A linear force transducer has an output of 20 mV when measuring 100 N and has an out of 100 mV when measuring 300 N. What is the zero offset error in mV?


___ (**numeric**) A linear displacement transducer reads 0 mm when measuring 0 mm and reads 110 mm when measuring 100 mm. What is the actual displacement when the transducer reads 385 mm?



___ Suppose $J_{reference} < 0^{\circ}C$. The voltage v in the diagram above will indicate a higher temperature at the sensing junction than is actually there.

Why or why not? _____

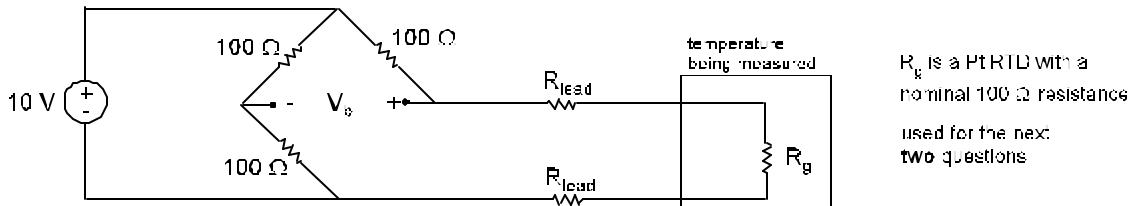
___ If the temperature of J_{sense} becomes lower than that of the $J_{reference}$, v will be negative.



___ A two-wire measurement is used in determining an RTD temperature. For $T > 0^{\circ}C$, $V_b > 0$.

Why or why not? _____

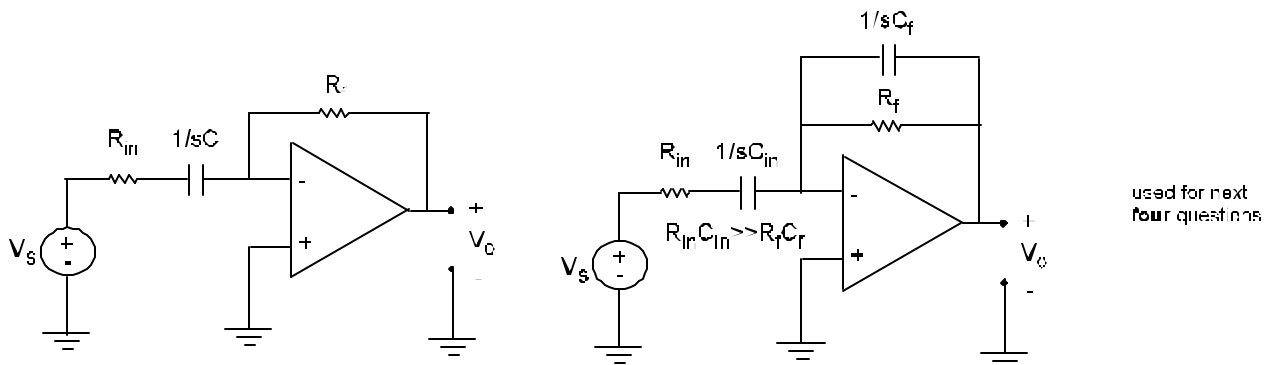___ The presence of lead resistance will tend to cause V_b to indicate too high a temperature.



___ Increasing C in the *high-pass* filter will lower its break frequency.

___ Increasing R_{in} in the *bandpass* filter has no effect on its lower break frequency .

___ Increasing C in the *high-pass* filter has no effect on its high-frequency gain.

___ Increasing C_{in} in the *bandpass* filter has no effect on its passband gain.